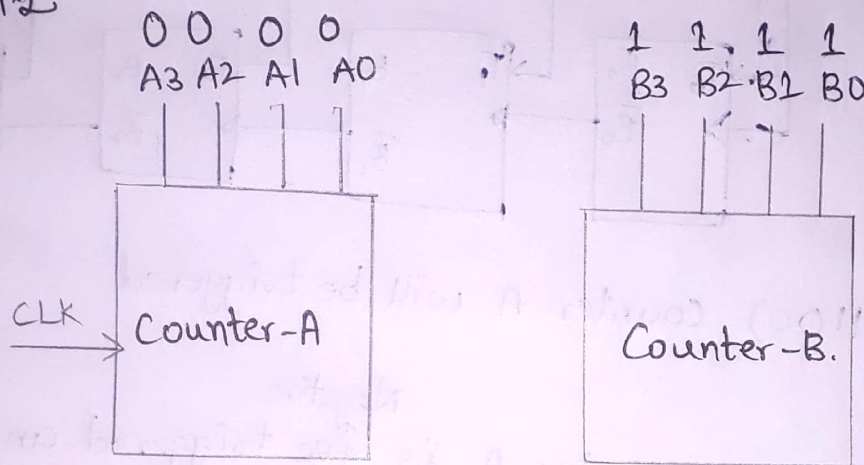


## Assignment.

These are: 2 Counters, "Counter-A" being asynchronous up counter & "Counter-B" is an asynchronous down counter and at  $T=0$ , 0000 & 1111 are loaded respectively as shown. clock source (CLK) available is

1MHz




1. Complete the design such that Counter B decrements by One value each time when decimal "12" appears at output of Counter A (A0 being LSB)?

a) find the no. of flipflops required

$$\log_2 16 = 4$$

 b) Consider any type of flipflop here I am considering T-flipflop.








approximately counter B repeats 12 times. So

In counter B when a value decrements 12 times then it is equal 0011 (3)

 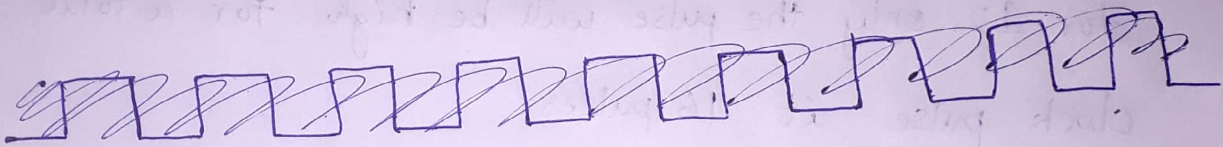
The counter A is a up counter so the decimal value of that is 7 (0111)



Clock pulses of Counter A

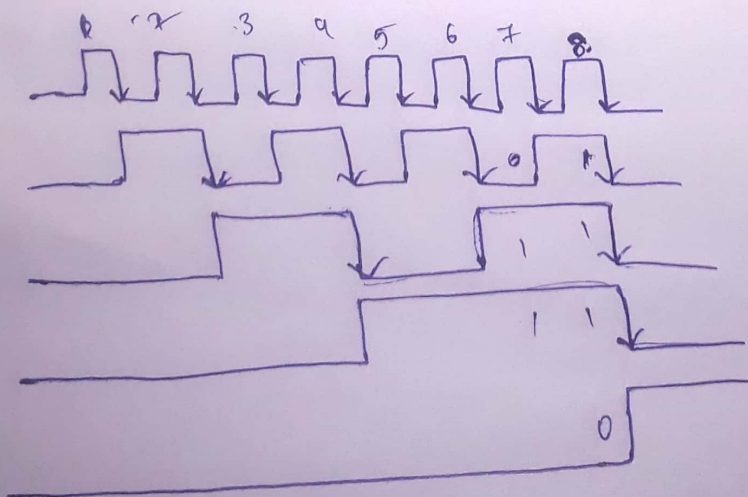

 3. What is the frequency of B0 with respect to clk (1MHz)?



For 12 only the pulse will be high for a total clock pulse it 16 pulses

Time of the 1MHz = 1μs .. So 16 × 1μs  
= 16μs

$$= \frac{1}{16\mu s} = \frac{1}{16 \times 10^{-6}} = 0.0625 \text{ MHz}$$

$$= 62.5 \text{ KHz}$$

$$= \frac{62.5}{2} = 31.25$$