

Verilog Code

```
// non overlapping of 1011 mealy machine
module mealy1011(input rst,clk,in,output reg out);

    reg [1:0] state;

    parameter s0=0,s1=1,s2=2,s3=3;

    always @(posedge clk) begin

        if(rst) begin

            out=0;

            state=s0;

        end

        else

            case(state)

                s0: begin

                    if(in)

                        state=s1;

                    else

                        state=s0;

                    out=0;

                end

                s1: begin

                    if(in)

                        state=s1;

                    else

                        state=s2;

                    out=0;

                end

                s2: begin
```

```

        if(in)
            state=s3;
        else
            state=s0;
        out=0;
    end

s3: begin
    if(in) begin
        state=s0;
        out=1;
    end
    else begin
        state=s2;
        out=0;
    end
end

endcase

end

endmodule

```

Testbench

```

module mealy1011_test();

    reg rst,clk,in;

    wire out;

    initial begin

        // Dump waves

```

```
$dumpfile("dump.vcd");  
$dumpvars(0);  
end  
  
    mealy1011 DUT(rst,clk,in,out);  
  
    initial begin  
  
        clk=0;in=0;  
  
        rst=1; #40;  
  
        rst=0;  
  
        in=0;#20;  
  
        in=1;#20;  
  
        in=0;#20;  
  
        in=1;#20;  
  
        in=1;#20;  
  
        in=0;#20;  
  
        in=1;#20;  
  
        in=1;#20;  
  
        in=0;#20;  
  
        in=0;#20;  
  
        in=1;#20;  
  
        in=0;#20;  
  
        in=1;#20;  
  
        in=1;#20;  
  
        $finish;  
  
    end  
  
    always #10 clk=!clk;  
  
endmodule
```



```
begin
    if(reset)
        PS <= S0;
    else
        PS <= NS ;
    end
always @(PS, x)
begin
case(PS)
    S0 : begin
        NS = x ? S1 : S0 ;
        $display(PS);
    end
    S1 : begin
        NS = x ? S1 : S2 ;
        $display(PS);
    end
    S2 : begin
        NS = x ? S3 : S0 ;
        $display(PS);
    end
    S3 : begin
        NS = x ? S4 : S2 ;
        $display(PS);
    end
    S4 : begin
        NS = x ? S1 : S2 ;
```

```
$display(PS);  
  
end  
  
default: NS = S0;  
  
endcase  
  
end  
  
always @(PS)  
  
begin  
  
    case(PS)  
  
        S4: z = 1;  
  
        default: z = 0;  
  
    endcase  
  
end  
  
endmodule
```

Testbench

```
module testbench;  
  
    // Inputs  
  
    reg x;  
  
    reg clk;  
  
    reg reset;  
  
    // Outputs  
  
    wire z;  
  
    seq_detector uut (.x(x), .clk(clk), .reset(reset), .z(z));  
  
  
    always #5 clk = ~ clk;  
  
  
    initial begin  
  
        $dumpfile("dump.vcd");
```

```
$dumpvars(1, testbench);
```

```
fork
```

```
clk = 1'b0;
```

```
reset = 1'b1;
```

```
#15 reset = 1'b0;
```

```
begin
```

```
#12 x = 0;#10 x = 0 ; #10 x = 1 ; #10 x = 0 ;
```

```
#12 x = 1;#10 x = 1 ; #10 x = 0 ; #10 x = 1 ;
```

```
#12 x = 1;#10 x = 0 ; #10 x = 0 ; #10 x = 1 ;
```

```
#12 x = 0;#10 x = 1 ; #10 x = 1 ; #10 x = 0 ;
```


```
#10 $finish;
```

```
end
```

```
join
```

```
end
```


```
endmodule
```

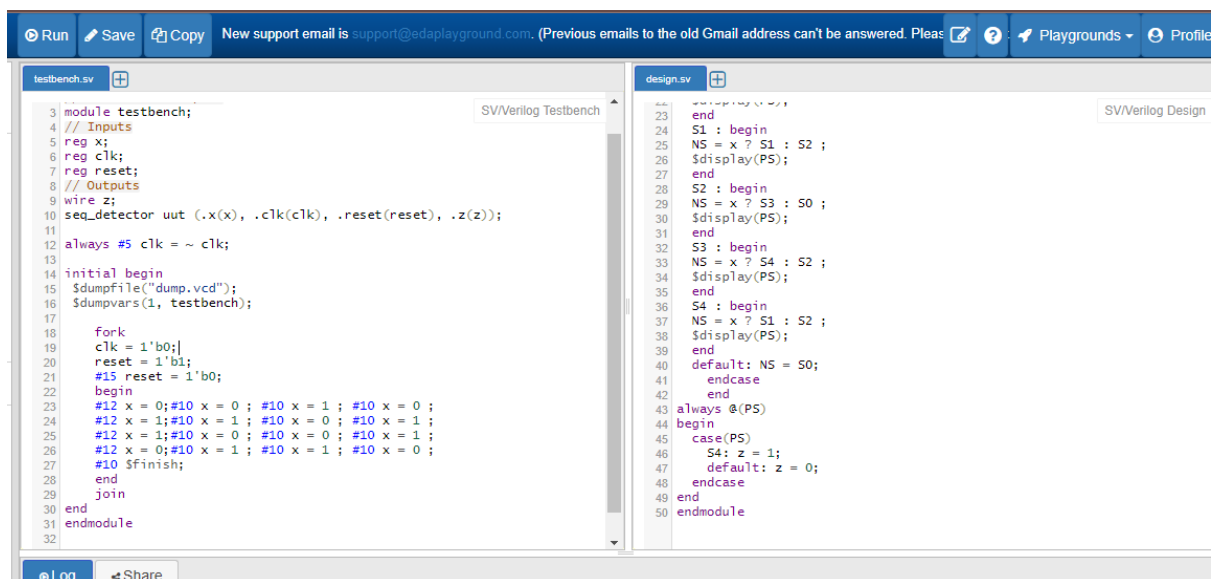

The screenshot shows a Verilog IDE with two files: testbench.v and design.v. The testbench.v file contains a module testbench with inputs x, clk, and reset, and output z. It includes a fork block with a begin block containing timing delays and signal assignments for x, and a join block. The design.v file contains a module design with a case statement for z, which is connected to the output of the testbench module. The IDE interface includes a top toolbar with Run, Save, Copy, and a message about support email, and a bottom toolbar with Log and Share buttons.

```
3 module testbench;
4 // Inputs
5 reg x;
6 reg clk;
7 reg reset;
8 // Outputs
9 wire z;
10 seq_detector uut (.x(x), .clk(clk), .reset(reset), .z(z));
11
12 always #5 clk = ~ clk;
13
14 initial begin
15 $dumpfile("dump.vcd");
16 $dumpvars(1, testbench);
17
18 fork
19   clk = 1'b0;
20   reset = 1'b1;
21   #15 reset = 1'b0;
22   begin
23     #12 x = 0;#10 x = 0 ; #10 x = 1 ; #10 x = 0 ;
24     #12 x = 1;#10 x = 1 ; #10 x = 0 ; #10 x = 1 ;
25     #12 x = 1;#10 x = 0 ; #10 x = 0 ; #10 x = 1 ;
26     #12 x = 0;#10 x = 1 ; #10 x = 1 ; #10 x = 0 ;
27     #10 $finish;
28   end
29 join
30 end
31 endmodule
32
```

```
23 end
24 S1 : begin
25   NS = x ? S1 : S2 ;
26   $display(P5);
27 end
28 S2 : begin
29   NS = x ? S3 : S0 ;
30   $display(P5);
31 end
32 S3 : begin
33   NS = x ? S4 : S2 ;
34   $display(P5);
35 end
36 S4 : begin
37   NS = x ? S1 : S2 ;
38   $display(P5);
39 end
40 default: NS = S0;
41 endcase
42 end
43 always @(P5)
44 begin
45   case(P5)
46     S4: z = 1;
47     default: z = 0;
48   endcase
49 end
50 endmodule
```

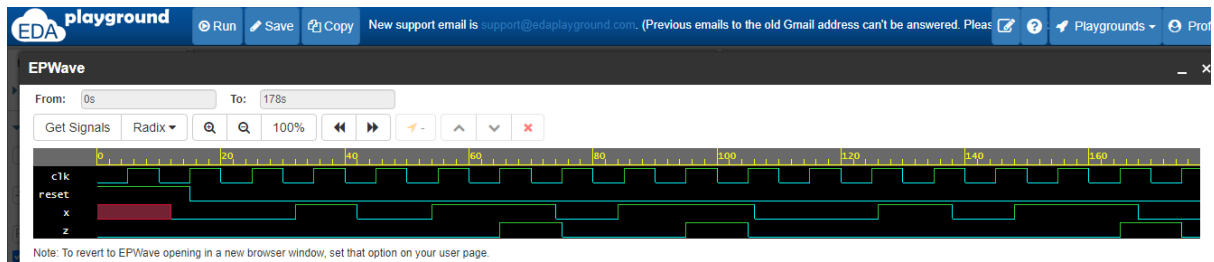

Verilog Code for Asynchronous Counters

```
module counter1(input wire clk,  
  
    output reg [3:0] count_A,  
  
        output reg [3:0] count_B);  
  
    reg [3:0] load_a;  
    reg [3:0] load_b;  
  
    always @(posedge clk) begin  
  
        if (count_A == 4'b1100)  
            count_B <= count_B - 1;  
            count_A <= count_A + 1;  
  
    end  
  
    initial begin  
  
        load_a = 4'b0000;  
        load_b = 4'b1111;  
  
        count_A <= load_a;  
        count_B <= load_b;  
  
    end  
  
endmodule
```


Testbench

```
module tb;

reg clk;

reg [3:0] count_A, count_B;

// Instantiate the asynchronous_counters module
counter1 uut (

    .clk(clk),

    .count_A(count_A),

    .count_B(count_B)

);


// Clock generation

initial begin

    clk = 0;

    forever #0.5 clk = ~clk; // 1MHz clock frequency

end


// Simulation for 200 clock cycles

initial begin

    #200 $finish;

end


// Display the results

always @(posedge clk) begin

    $display("Time = %0d :Counter A = %d, Counter B = %d", $time, count_A, count_B);

end

endmodule
```

```
1 // Code your testbench here
2 // or browse Examples
3 module tb;
4
5   reg clk;
6   reg [3:0] count_A, count_B;
7
8   // Instantiate the asynchronous_counters module
9   counter1 uut (
10     .clk(clk),
11     .count_A(count_A),
12     .count_B(count_B)
13   );
14
15   // Clock generation
16   initial begin
17     clk = 0;
18     forever #0.5 clk = ~clk; // 1MHz clock frequency
19   end
20
21   // Simulation for 200 clock cycles
22   initial begin
23     #200 $finish;
24   end
25
26   // Display the results
27   always @(posedge clk) begin
28     $display("Time = %t: Counter A = %d, Counter B = %d", $time,
29             count_A, count_B);
30   end
31 endmodule
```

```
1 // Code your design here
2 module counter1(input wire clk,
3   output reg [3:0] count_A,
4   output reg [3:0] count_B);
5
6   reg [3:0] load_a;
7   reg [3:0] load_b;
8   always @(posedge clk) begin
9     if (count_A == 4'b1100)
10       count_B <= count_B - 1;
11     count_A <= count_A + 1;
12   end
13
14   initial begin
15     load_a = 4'b0000;
16     load_b = 4'b1111;
17
18     count_A <= load_a;
19     count_B <= load_b;
20   end
21 endmodule
```

```
3 module tb;
4
5   reg clk;
6   reg [3:0] count_A, count_B;
7
8   // Instantiate the asynchronous_counters module
9   counter1 uut (
10     .clk(clk),
11     .count_A(count_A),
12     .count_B(count_B)
13   );
14
15   // Clock generation
16   initial begin
17     clk = 0;
18     forever #0.5 clk = ~clk; // 1MHz clock frequency
19   end
20
21   // Simulation for 200 clock cycles
22   initial begin
23     #200 $finish;
24   end
25
26   // Display the results
27   always @(posedge clk) begin
28     $display("Time = %t: Counter A = %d, Counter B = %d", $time,
29             count_A, count_B);
30   end
31 endmodule
```

```
1 // Code your design here
2 module counter1(input wire clk,
3   output reg [3:0] count_A,
4   output reg [3:0] count_B);
5
6   reg [3:0] load_a;
7   reg [3:0] load_b;
8   always @(posedge clk) begin
9     if (count_A == 4'b1100)
10       count_B <= count_B - 1;
11     count_A <= count_A + 1;
12   end
13
14   initial begin
15     load_a = 4'b0000;
16     load_b = 4'b1111;
17
18     count_A <= load_a;
19     count_B <= load_b;
20   end
21 endmodule
```

```
[2024-01-22 12:36:56 UTC] iverilog '-Wall' '-g2012' design.sv testbench.sv && unbuffer vvp a.out
Time = 1: Counter A = 0, Counter B = 15
Time = 3: Counter A = 1, Counter B = 15
Time = 5: Counter A = 2, Counter B = 15
Time = 7: Counter A = 3, Counter B = 15
Time = 9: Counter A = 4, Counter B = 15
Time = 11: Counter A = 5, Counter B = 15
Time = 13: Counter A = 6, Counter B = 15
Time = 15: Counter A = 7, Counter B = 15
Time = 17: Counter A = 8, Counter B = 15
Time = 19: Counter A = 9, Counter B = 15
Time = 21: Counter A = 10, Counter B = 15
Time = 23: Counter A = 11, Counter B = 15
Time = 25: Counter A = 12, Counter B = 15
Time = 27: Counter A = 13, Counter B = 14
Time = 29: Counter A = 14, Counter B = 14
Time = 31: Counter A = 15, Counter B = 14
```

Verilog Code for Even priority encoder

module prioritygen(input [3:0] ip,output reg[3:0] op);

always @ (*) begin

case(ip)

4'b0000: op = 4'b0000;

4'b0001: op = 4'b0000;

4'b0010: op = 4'b0010;

4'b0011: op = 4'b0010;

```
4'b0100: op = 4'b0100;
4'b0101: op = 4'b0100;
4'b0110: op = 4'b0110;
4'b0111: op = 4'b0110;
4'b1000: op = 4'b1000;
4'b1001: op = 4'b1000;
4'b1010: op = 4'b1010;
4'b1011: op = 4'b1010;
4'b1100: op = 4'b1100;
4'b1101: op = 4'b1100;
4'b1110: op = 4'b1110;
4'b1111: op = 4'b1110;
```

```
endcase
```

```
end
```

```
endmodule
```

Testbench

```
module tb;

reg [3:0] ip;

wire [3:0] op;

prioritygen uut (.ip(ip),.op(op));

reg clk = 0;

always #5 clk = ~clk;

initial begin

    ip = 4'b0010;

    #10;

    ip = 4'b1001;

    #10;
```

```

ip = 4'b0111;

#10;

$finish;

end


always @(posedge clk) begin

    $display("Time = %0t: ip = %b, op = %b", $time, ip, op);

end

endmodule

```

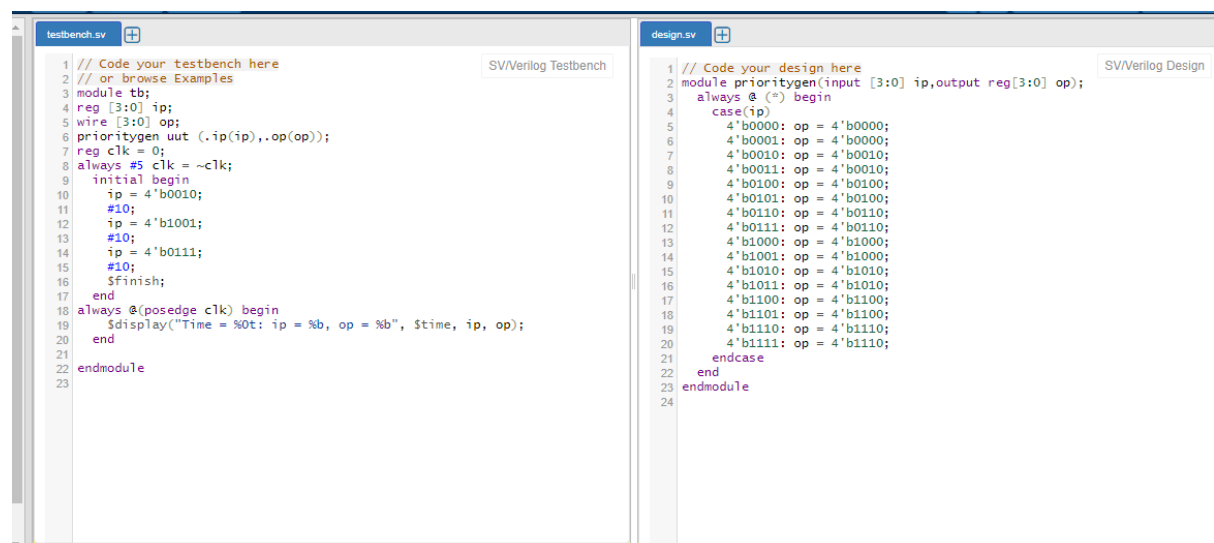


```

testbench.v
1 // Code your testbench here
2 // or browse Examples
3 module tb;
4 reg [3:0] ip;
5 wire [3:0] op;
6 prioritygen uut (.ip(ip),.op(op));
7 reg clk = 0;
8 always #5 clk = ~clk;
9 initial begin
10 ip = 4'b0010;
11 #10;
12 ip = 4'b1001;
13 #10;
14 ip = 4'b0111;
15 #10;
16 $finish;
17 end
18 always @(posedge clk) begin
19 $display("Time = %0t: ip = %b, op = %b", $time, ip, op);
20 end
21 endmodule
22
23

design.v
1 // Code your design here
2 module prioritygen(input [3:0] ip,output reg[3:0] op);
3 always @ (*) begin
4 case(ip)
5 4'b0000: op = 4'b0000;
6 4'b0001: op = 4'b0000;
7 4'b0010: op = 4'b0010;
8 4'b0011: op = 4'b0010;
9 4'b0100: op = 4'b0100;
10 4'b0101: op = 4'b0100;
11 4'b0110: op = 4'b0110;
12 4'b0111: op = 4'b0110;
13 4'b1000: op = 4'b1000;
14 4'b1001: op = 4'b1000;
15 4'b1010: op = 4'b1010;
16 4'b1011: op = 4'b1010;
17 4'b1100: op = 4'b1100;
18 4'b1101: op = 4'b1100;
19 4'b1110: op = 4'b1110;
20 4'b1111: op = 4'b1110;
21 endcase
22 end
23 endmodule
24

```

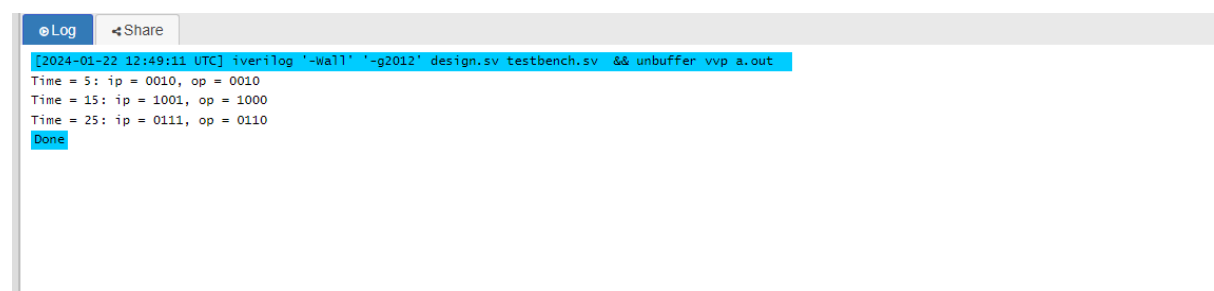

```

Log
[2024-01-22 12:49:11 UTC] iverilog '-wall' '-g2012' design.v testbench.v && unbuffer vvp a.out
Time = 5: ip = 0010, op = 0010
Time = 15: ip = 1001, op = 1000
Time = 25: ip = 0111, op = 0110
Done

```

Verilog Code for 3-bit Multiplier using Shift register

```

module multiplier_3bit(A, B, P);

input [2:0] A, B;

output [5:0] P;

```

```
wire [5:0] products [2:0];

assign products[0] = (B[0]) ? (A << 0) : 6'b0;

assign products[1] = (B[1]) ? (A << 1) : 6'b0;

assign products[2] = (B[2]) ? (A << 2) : 6'b0;


assign P = products[0] + products[1] + products[2];

endmodule
```

Testbench

```
module tb_multiplier_3bit_shift;

reg [2:0] A, B;

wire [5:0] P;

multiplier_3bit uut (.A(A),.B(B),.P(P));

reg clk;

always #5 clk = ~clk;

initial begin

    A = 3'b001;

    B = 3'b011;

    $monitor("Time=%0t A=%b B=%b P=%b", $time, A, B, P);

    #5 A = 3'b010;

    #5 B = 3'b101;


    #5 A = 3'b110;

    #5 B = 3'b011;

    #10 $finish;

end

endmodule
```

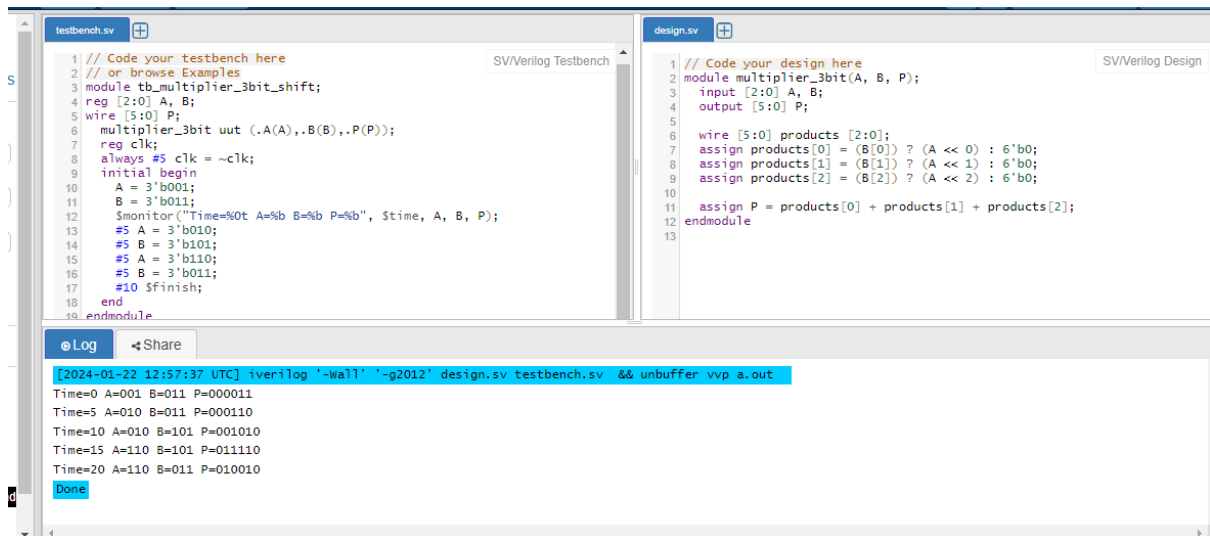

Verilog Code for counting of rising and falling edges and total count

module risingandfalling (

input clk,

input reset,

input signal,

output reg rising_edge,

output reg falling_edge,

output reg [7:0] edge_count

);

reg prev_signal;

always @(posedge clk or posedge reset) begin

if (reset) begin

prev_signal <= 0;

rising_edge <= 0;

falling_edge <= 0;

edge_count <= 0;

end else begin

prev_signal <= signal;

```

    rising_edge <= (signal & ~prev_signal);
    falling_edge <= (~signal & prev_signal);

    if (rising_edge | falling_edge) begin
        edge_count <= edge_count + 1;
    end

end

endmodule

Testbench

module tb;

    reg clk, reset, signal;

    wire rising_edge, falling_edge;

    wire [7:0] edge_count;

    risingandfalling dut (.clk(clk),.reset(reset),.signal(signal),
        .rising_edge(rising_edge),.falling_edge(falling_edge),
        .edge_count(edge_count));

    initial begin
        $dumpfile("dump.vcd");
        $dumpvars;
    end

    initial begin
        clk = 1'b0;

        forever #5 clk = ~clk;
    end

end

```

```
initial begin
```

```
    reset = 1'b1;
```

```
    #10 reset = 1'b0;
```

```
    #10 signal = 1'b1;
```

```
    #10 signal = 1'b0;
```

```
    #10 signal = 1'b1;
```

```
    #20 signal = 1'b0;
```

```
    #10 signal = 1'b1;
```

```
    #5 signal = 1'b0;
```

```
    #5 signal = 1'b1;
```

```
    #5 signal = 1'b0;
```

```
    #5 signal = 1'b1;
```

```
    #10 $finish;
```

```
end
```

```
initial begin
```

```
    $monitor("At time %t, clk = %b, reset = %b, signal = %b, rising_edge = %b, falling_edge = %b,  
edge_count = %d",
```

```
        $time, clk, reset, signal, rising_edge, falling_edge, edge_count);
```


```
end
```

```
endmodule
```


testbench.vv | design.vv

Log | Share

At time 10, clk = 0, reset = 0, signal = x, rising_edge = 0, falling_edge = 0, edge_count = 0
At time 15, clk = 1, reset = 0, signal = x, rising_edge = x, falling_edge = 0, edge_count = 0
At time 20, clk = 0, reset = 0, signal = 1, rising_edge = x, falling_edge = 0, edge_count = 0
At time 25, clk = 1, reset = 0, signal = 1, rising_edge = x, falling_edge = 0, edge_count = 0
At time 30, clk = 0, reset = 0, signal = 0, rising_edge = x, falling_edge = 0, edge_count = 0
At time 35, clk = 1, reset = 0, signal = 0, rising_edge = 0, falling_edge = 1, edge_count = 0
At time 40, clk = 0, reset = 0, signal = 1, rising_edge = 0, falling_edge = 1, edge_count = 0
At time 45, clk = 1, reset = 0, signal = 1, rising_edge = 1, falling_edge = 0, edge_count = 1
At time 50, clk = 0, reset = 0, signal = 1, rising_edge = 1, falling_edge = 0, edge_count = 1
At time 55, clk = 1, reset = 0, signal = 1, rising_edge = 0, falling_edge = 0, edge_count = 2
At time 60, clk = 0, reset = 0, signal = 0, rising_edge = 0, falling_edge = 0, edge_count = 2
At time 65, clk = 1, reset = 0, signal = 0, rising_edge = 0, falling_edge = 1, edge_count = 2
At time 70, clk = 0, reset = 0, signal = 1, rising_edge = 0, falling_edge = 1, edge_count = 2
At time 75, clk = 1, reset = 0, signal = 0, rising_edge = 0, falling_edge = 0, edge_count = 3
At time 80, clk = 0, reset = 0, signal = 1, rising_edge = 0, falling_edge = 0, edge_count = 3
At time 85, clk = 1, reset = 0, signal = 0, rising_edge = 0, falling_edge = 0, edge_count = 3
At time 90, clk = 0, reset = 0, signal = 1, rising_edge = 0, falling_edge = 0, edge_count = 3
At time 95, clk = 1, reset = 0, signal = 1, rising_edge = 1, falling_edge = 0, edge_count = 3
At time 100, clk = 0, reset = 0, signal = 1, rising_edge = 1, falling_edge = 0, edge_count = 3
Finding VCD file...
./dump.vcd
[2024-01-22 13:15:56 UTC] Opening EPWave...
Done

 

Note: To revert to EPWave opening in a new browser window, set that option on your user page.