
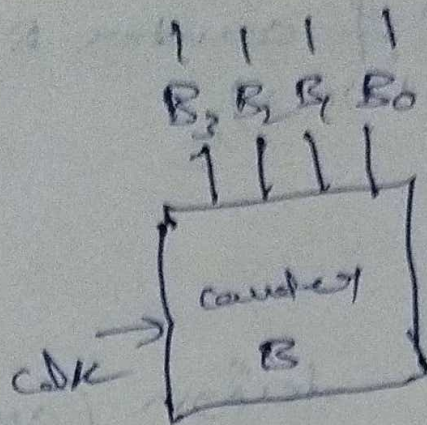



# Ques

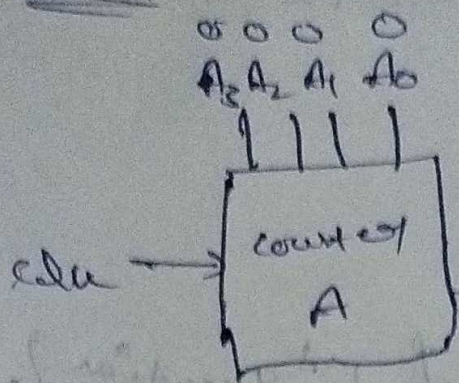

→ The counter "A" is loaded with "0000" and it is an asynchronous up counter. and Counter B is an asynchronous down counter and loaded with "1111".



→ The counter B decrements when the output of counter "A" is 12.

12 →  $A_3 A_2 A_1 A_0$   
1100

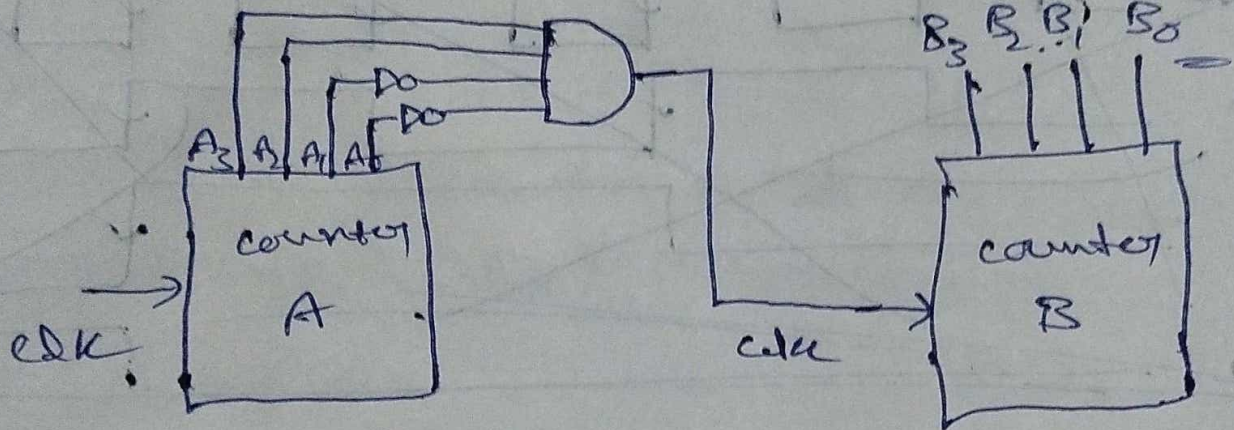

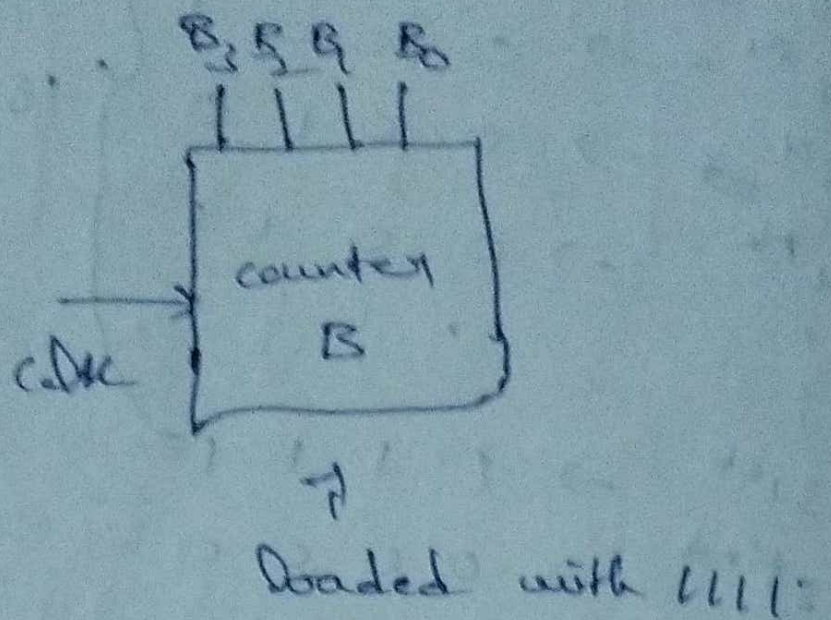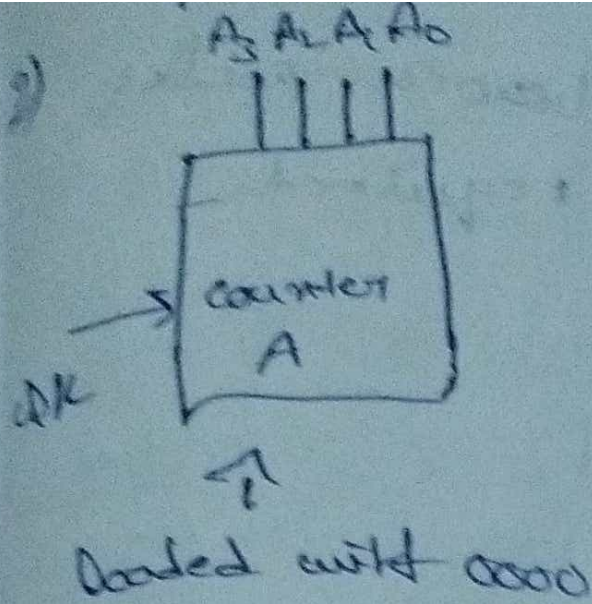
⇒ Here, clock of counter B is active when the output of counter A is 12.





Frequency of clock source = 1 MHz.
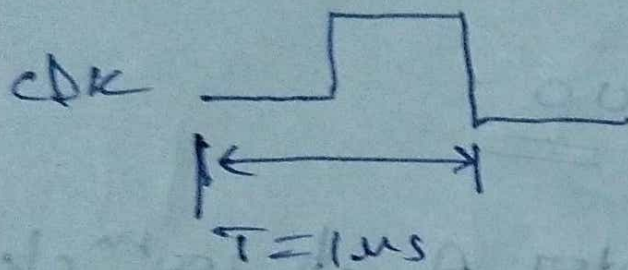
$$T = \frac{1}{f} = \frac{1}{1 \times 10^6} = 1 \mu\text{sec}$$



So, The decimal values at o/p of both counters A & B at  $T = 0.2 \text{ ms}$  is,

$$\text{no. of clock pulses} = \frac{0.2 \times 10^{-3}}{1 \times 10^{-6}} = 0.2 \times 10^3 = 200$$

→ In counter A,

Initial → 0 0 0 0  
 1<sup>st</sup> clk → 0 0 0 1  
 2<sup>nd</sup> clk → 0 0 1 0  
 ⋮  
 15<sup>th</sup> clk → 1 1 1 1

→ 15 clock pulses required to complete all states



$16^{\text{th}}$  clck  $\rightarrow 0 \ 0 \ 0 \ 0$   
 $17^{\text{th}}$  "  $\rightarrow 0 \ 0 \ 0 \ 1$   
 $18^{\text{th}}$  "  $\rightarrow 0 \ 0 \ 1 \ 0$   
 $19^{\text{th}}$  "  $\rightarrow 0 \ 0 \ 1 \ 1$   
 $\vdots$   
 $31^{\text{st}}$  "  $\rightarrow 1 \ 1 \ 1 \ 1$   
 $32^{\text{nd}}$  "  $\rightarrow 0 \ 0 \ 0 \ 0$

16 clcks. needed required.

$$\therefore 20 - 15 = \frac{185}{16} = 11 \text{ \& remainder } = 9$$

$192^{\text{nd}}$  clck  $\rightarrow 0 \ 0 \ 0 \ 0$   
 $193^{\text{rd}}$  "  $\rightarrow 0 \ 0 \ 0 \ 1$

$200^{\text{th}}$  clck  $\rightarrow 1 \ 0 \ 0 \ 0$

$\therefore$  The o/p of counter A at  $200^{\text{th}}$  clck pulse is  $1000 \rightarrow (8)_{10}$

For counter B

$\rightarrow$  The counter A completed 12 full circulation. So, counter B is decremented 12 times.

Initial  $\rightarrow 1 \ 1 \ 1 \ 1$        $5^{\text{th}}$   $\rightarrow 1 \ 0 \ 1 \ 0$   
 $1^{\text{st}}$   $\rightarrow 1 \ 1 \ 1 \ 0$        $6^{\text{th}}$   $\rightarrow 1 \ 0 \ 0 \ 1$   
 $2^{\text{nd}}$   $\rightarrow 1 \ 1 \ 0 \ 1$        $7^{\text{th}}$   $\rightarrow 1 \ 0 \ 0 \ 0$   
 $3^{\text{rd}}$   $\rightarrow 1 \ 1 \ 0 \ 0$        $\vdots$   
 $4^{\text{th}}$   $\rightarrow 1 \ 0 \ 1 \ 1$        $12^{\text{th}}$   $\rightarrow 0 \ 0 \ 1 \ 1$



→ The o/p of counter B after 12 decrements is 0011 (3)

3) After

From the design (answer of 1st question), The counter B is connected to counter A.

→ The freq. of B is :-

→ B follows A<sub>3</sub> output and B is the 5<sup>th</sup> flip flop.

$$f_{req. B} = \frac{f_{req. in}}{2^5} = \frac{1 \text{ MHz}}{32} = 31.25 \text{ kHz}$$