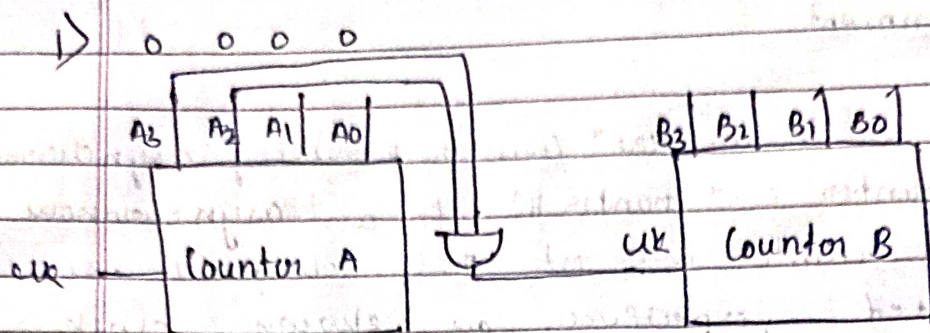


$$1100 = 12$$




Date : _____

Page No : _____



clk frequency = 1 MHz
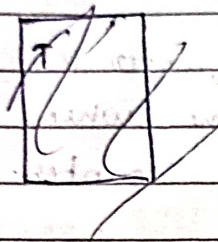
$$\text{Time period} = \frac{1}{1 \text{ MHz}} = 1 \times 10^{-6} \text{ s}$$



$$T = 1 \mu\text{s}$$

- 2) Counter A is a upcounter which counts from 0000 - 1111 which resets at 15. which requires 16 clock pulses.

At the 1100 state the clock pulse will be given to the counter B which will

which will have a time period of $16 \mu\text{s}$ and a frequency

$$\frac{1}{16 \mu\text{s}} = 0.0625 \times 10^6 \text{ Hz}$$

$$= 62.5 \text{ kHz}$$

$$\text{Now } 0.2 \text{ ms} = 200 \mu\text{s}, 0.2 \times 10^{-3} \text{ s}$$

$$\frac{0.2 \times 10^{-3}}{1 \times 10^{-6}} = 200$$

So at that instant of 0.2 ms



we will get 200 clock pulses.

counter A will reset at 16 clock pulses.
 $\therefore 200 \% 16 = 8$ (remainder).

~~counter B will reset at~~
 \therefore counter A will be at 0111 state
at $t = 0.2 \text{ ms}$.

~~counter B will reset at 12 clock pulses.~~

~~200 %~~

At every 1100 state we will give
clock pulse.

$$200 / 16 = 12.$$


We will give 12 clock pulses to Counter B.
~~1111~~ (12)


$$16 - 12 = 4$$

\therefore counter B will be at 0011 state at $t = 0.2 \text{ ms}$

counter B.

(3).

clk 
frequency = 62.5 kHz .

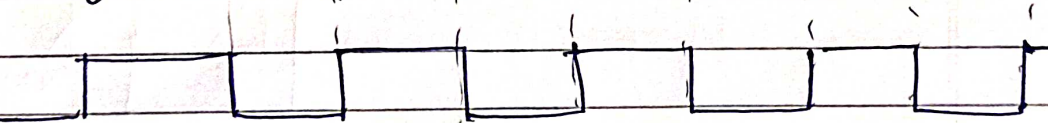B₀ 

$$\frac{62.5 \text{ kHz}}{2} = 31.25 \text{ kHz}$$

frequency of B₀ will be 31.25 kHz